MATHEMATICS

University *of* NORTH ALABAMA

Fall 2025 Math Problem of the Week: Problem #11

Due noon Monday, November 3
Open to all UNA undergraduates

Directions: Deliver your written solution to me (Dr. Bryant) in CPTMTH 328 by noon Monday, November 3 or, if you cannot find me, you may leave it with Ms. Phifer in CPTMTH 377. All work must be your own. You are required to justify your response fully. If you utilize a well-known theorem, state the theorem's full name and proposition, showing that the conditions of the theorem are met. Good luck!

Problem #10: Consider the graph of an n-cube having 2^n vertices $(\pm 1, \pm 1, \ldots, \pm 1)$, with edges joining each pair of vertices that differ in just one-coordinate.

(a) If each edge is a 1-ohm resistor, find the resistance between vertices $(-1, -1, \ldots, -1)$ and $(1, 1, \ldots, 1)$.

(b) What happens to the resistance as $n \to \infty$?